

## Example of solving RC circuit by Laplace transform

Consider a series RC circuit with a known time dependent input voltage  $V(t)$ . We will determine the charge  $Q$  on the capacitor as a function of time. The charge is governed by the following differential equation.

$$V(t) = R \frac{dQ}{dt} + \frac{1}{C}Q$$

Taking a Laplace transform of both sides we get

$$\begin{aligned} L\{V\}(s) &= RL \left\{ \frac{dQ}{dt} \right\} (s) + \frac{1}{C}L\{Q\}(s) \\ &= R(-Q(0) + sL\{Q\}(s)) + \frac{1}{C}L\{Q\}(s) \\ &= -RQ(0) + (Rs + 1/C)L\{Q\}(s) \\ \implies L\{Q\}(s) &= \frac{L\{V\}(s) + RQ(0)}{Rs + 1/C} \end{aligned}$$

We can now recover the charge as a function of time by inverting the Laplace transform. Here is a table of the inverse Laplace transforms we will use in this example:

$Y(s)$	$L^{-1}\{Y\}(t)$
$\frac{1}{s-a}$	$e^{at}$
$\frac{1}{s}e^{-as}$	$u_a(t)$
$e^{-as}Y(s)$	$u_a(t)L^{-1}\{Y\}(t-a)$

### Case 1: Input voltage is zero

In this case,

$$\begin{aligned} L\{Q\}(s) &= \frac{RQ(0)}{Rs + 1/C} \\ &= \frac{Q(0)}{s - (-1/RC)}. \end{aligned}$$

Now take an inverse Laplace transform. We use the first row of our inverse transform table with  $a = -1/RC$ .

$$\begin{aligned} \implies Q(t) &= Q(0)L^{-1} \left\{ \frac{1}{s - (-1/RC)} \right\} \\ &= Q(0)e^{-t/RC}. \end{aligned}$$

### Case 2: Input voltage is unit step function

Now let's suppose that the input voltage is a unit step function at some time  $\tau$ . The Laplace transform of this step function is

$$L\{u_\tau\}(s) = \frac{1}{s}e^{-\tau s},$$

So our equation for the Laplace transform of  $Q$  becomes

$$\begin{aligned} L\{Q\}(s) &= \frac{e^{-\tau s}/s + RQ(0)}{Rs + 1/C} \\ &= e^{-\tau s} \frac{1}{s(Rs + 1/C)} + \frac{Q(0)}{s - (-1/RC)} \end{aligned}$$

Notice that we already took the inverse transform of the second term when we solved the problem with  $V(t) = 0$ . Take an inverse Laplace transform; use the  $V(t) = 0$  solution; then apply the third rule in our table:

$$\begin{aligned} Q(t) &= L^{-1} \left\{ e^{-\tau s} \frac{1}{s(Rs + 1/C)} \right\} + L^{-1} \left\{ \frac{Q(0)}{s - (-1/RC)} \right\} \\ &= L^{-1} \left\{ e^{-\tau s} \frac{1}{s(Rs + 1/C)} \right\} + Q(0)e^{(-1/RC)t} \\ &= u_{\tau}(t)L^{-1} \left\{ \frac{1}{s(Rs + 1/C)} \right\} (t - \tau) + Q(0)e^{(-1/RC)t} \end{aligned}$$

Almost done— do a partial fraction decomposition, then finish inverse transform using first rule in table.

$$\begin{aligned} \frac{1}{s(Rs + 1/C)} &= \frac{C}{s} - \frac{C}{s - (-1/RC)} \\ \Rightarrow L^{-1} \left\{ \frac{1}{s(Rs + 1/C)} \right\} &= CL^{-1} \left\{ \frac{1}{s} \right\} - CL^{-1} \left\{ \frac{1}{s - (-1/RC)} \right\} \\ &= Ce^0 - Ce^{(-1/RC)t} \\ &= C - Ce^{-t/RC} \end{aligned}$$

Done. We have calculated the following formula for the charge as a function of time:

$$\begin{aligned} Q(t) &= u_{\tau}(t)L^{-1} \left\{ \frac{1}{s(Rs + 1/C)} \right\} (t - \tau) + Q(0)e^{(-1/RC)t} \\ &= u_{\tau}(t) \left( C - Ce^{-(t-\tau)/RC} \right) + Q(0)e^{-t/RC} \end{aligned}$$

### Example of solving underdamped LRC circuit by Laplace transform

Now let's add an inductor, so that we have a series LRC circuit. Since we've been using  $L$  for the Laplace transform operator, we will denote the inductance of our circuit with a lowercase  $l$ . The voltage equation now reads

$$V(t) = l \frac{d^2 Q}{dt^2} + R \frac{dQ}{dt} + \frac{1}{C} Q$$

Taking a Laplace transform, we have

$$\begin{aligned} L\{V\}(s) &= l(-Q'(0) - sQ(0) + s^2 L\{Q\}(s)) + R(-Q(0) + sL\{Q\}(s)) + \frac{1}{C} L\{Q\}(s) \\ &= -(ls + R)Q(0) - lQ'(0) + (ls^2 + Rs + 1/C)L\{Q\}(s) \end{aligned}$$

It's easy to solve for the Laplace transform of  $Q$ .

$$L\{Q\}(s) = \frac{L\{V\}(s) + (s + R/l)Q(0) + Q'(0)}{(s^2 + Rs/l + 1/lC)}$$

### Case 1: Input voltage is zero

We'll need a few more entries in our Laplace transform table:

$Y(s)$	$L^{-1}\{Y\}(t)$
$\frac{s-a}{(s-a)^2+b^2}$	$e^{at} \cos(bt)$
$\frac{b}{(s-a)^2+b^2}$	$e^{at} \sin(bt)$

We can “complete the square” to make express our function in terms of quantities appearing in our inverse Laplace transform table. Let's assume that  $\frac{1}{lC} > \left(\frac{R}{2l}\right)^2$  so that we can take a real number square root in the following calculation. In this case, the circuit is said to be underdamped; this condition is sometimes expressed as  $\frac{R}{2} \sqrt{\frac{C}{l}} < 1$  (these conditions are equivalent).

$$\begin{aligned} L\{Q\}(s) &= \frac{(s+R/l)Q(0) + Q'(0)}{(s^2 + Rs/l + 1/lC)} \\ &= \frac{(s+R/l)Q(0) + Q'(0)}{(s-R/2l)^2 - (R/2l)^2 + 1/lC} \\ &= Q(0) \frac{(s+\frac{R}{2l})}{(s-\frac{R}{2l})^2 + \left(\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}\right)^2} + \frac{Q'(0) + \frac{R}{2l}Q(0)}{\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}} \frac{\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}}{(s-\frac{R}{2l})^2 + \left(\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}\right)^2}. \end{aligned}$$

Now take an inverse Laplace transform.

$$\begin{aligned} Q(t) &= Q(0)L^{-1}\left\{\frac{s-A}{(s-A)^2+B^2}\right\} + \frac{Q'(0) + \frac{R}{2l}Q(0)}{\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}} L^{-1}\left\{\frac{B}{(s-A)^2+B^2}\right\} \\ &= Q(0)e^{At} \cos(Bt) + \frac{Q'(0) + \frac{R}{2l}Q(0)}{\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}} e^{At} \sin(Bt) \end{aligned}$$

Finally, we have calculated  $Q(t)$ .

$$Q(t) = Q(0)e^{-(R/2l)t} \cos\left(t\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}\right) + \frac{Q'(0) + \frac{R}{2l}Q(0)}{\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}} e^{-(R/2l)t} \sin\left(t\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}\right)$$

### Case 1: Arbitrary input voltage

Recall the convolution formula for the inverse Laplace transform of a product. If  $L\{f\} = F$  and  $L\{g\} = G$ , then

$$L^{-1}\{F(s)G(s)\} = [u_0(t)f(t)] * [u_0(t)g(t)]$$

The square parenthesis are just indicating order of operations. We solve using an inverse Laplace transform.

$$\begin{aligned} L\{Q\}(s) &= \frac{L\{V\}(s) + (s+R/l)Q(0) + Q'(0)}{s^2 + Rs/l + 1/lC} \\ \implies Q(t) &= L^{-1}\left\{L\{V\}(s) \frac{1}{s^2 + Rs/l + 1/lC}\right\} + L^{-1}\left\{\frac{(s+R/l)Q(0) + Q'(0)}{s^2 + Rs/l + 1/lC}\right\} \\ &= [u_0(t)V(t)] * \left[u_0(t)L^{-1}\left\{\frac{1}{s^2 + Rs/l + 1/lC}\right\}\right] + L^{-1}\left\{\frac{(s+R/l)Q(0) + Q'(0)}{s^2 + Rs/l + 1/lC}\right\} \end{aligned}$$

We already calculated the second inverse transform in this formula. The first one is done similarly; we get

$$\begin{aligned}
 Q(t) = [u_0(t)V(t)] * & \left[ \frac{u_0(t)}{\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}} \sin \left( t \sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2} \right) \right] \\
 & + Q(0)e^{-(R/2l)t} \cos \left( t \sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2} \right) + \frac{Q'(0) + \frac{R}{2l}Q(0)}{\sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2}} e^{-(R/2l)t} \sin \left( t \sqrt{\frac{1}{lC} - \left(\frac{R}{2l}\right)^2} \right)
 \end{aligned}$$